

Problem Set #4

The due date for this homework is Tue 9 Apr 2013 12:59 PM EDT -0400.

Question 1

Single Cube Divisor Extraction from Multi-level Logic

Consider this Boolean logic network with variables a, b, c, d, e, f :

$$R = abf + abcd + abce + cdf$$


$$S = acd + cdef + abce$$

$$T = cdef + af$$

Build the *cube-literal matrix* associated with this set of functions. Look at what prime rectangles are possible in this matrix. Which are correct statements about extractions using this matrix?


- ☐ Single cube divisor cd can be extracted as a prime rectangle. It has 2 columns and 4 rows ($abcd, acd, cdef, cdf$). Extracting this divisor saves 3 literals.

 The picture below is a correct single-cube extraction based on a prime rectangle:



- ☐ Single cube divisor abc can be extracted as a prime rectangle. It has 3 columns, and 2 rows ($abcd, abce$). Extracting this divisor saves 3 literals.

 The picture below is a correct single-cube extraction based on a prime rectangle:



- ☐ Single cube divisor bc can be extracted as a prime rectangle which has 2 columns and 2 rows ($abcd, abce$). Extracting this divisor saves 3 literals.

Question 2

Multiple Cube Divisor Extraction from Multi-level Logic

Suppose we have these two Boolean functions, defined over 9 variables

$p, q, r, s, t, u, v, w, x$:

$$G = qt + rst + pqr + quvw + rsuvw$$

$$H = pu + qtx + qu + rsu$$

Use the ideas from the multiple-cube extraction methods from lecture, to build a *Co-kernel-Cube matrix*, and look for any good prime rectangles to extract a common divisor to reduce the complexity of the network.

To assist in this construction, here are all the kernels and co-kernels for these functions:

Function: $G = qt + rst + pqr + quvw + rsuvw$	
Kernel $t+pr+uvw$	co-kernel q
Kernel $t+uvw$	co-kernel rs
Kernel $st+pq+suvw$	co-kernel r
Kernel $q+rs$	co-kernel t
Kernel $q+rs$	co-kernel uvw
Function: $H = pu + qtx + qu + rsu$	
Kernel $u+tx$	co-kernel q
Kernel $p+q+rs$	co-kernel u

Which of the following are correct statements about this extraction process?

- ☐ Multiple-cube divisor $D = t + uvw$ can be extracted as a prime rectangle from this matrix. The prime rectangle has 2 columns and 2 rows: (Function Co-kernel) rows are: $(G \ q), (H \ u)$. This extraction saves 3 literals.

The picture below is a correct multi-cube extraction from this network.



- ☐ Before any common divisor extraction, the network with just the G and H nodes in it has 27 literals.

- ☐ Multiple-cube divisor $D = q + rs$ can be extracted as a prime rectangle from this matrix. The prime rectangle has 2 columns and 3 rows: (Function Co-kernel) rows are: $(G \ t)$, $(G \ uvw)$, $(H \ u)$. This extraction saves 8 literals.

- ☐ Multiple-cube divisor $D = q + tx$ can be extracted as a prime rectangle from this matrix. The prime rectangle has 2 columns and 3 rows: (Function Co-kernel) rows are: $(G \ q)$, $(G \ rs)$, $(H \ q)$. This extraction saves 4 literals.

Question 3

Basic Facts About Multi-Level Don't Cares

Which of these are correct statements about multi-level don't cares?


Select all the correct answers.

- ☐ Satisfiability Don't Cares (SDCs) are associated with wires inside a Boolean network model, and represent impossible patterns of inputs to, and the output of internal nodes.
- ☐ Multi-level don't cares are called "implicit" because they arise from the structure of a Boolean network model, and we need to go find them.
- ☐ Observability Don't Cares (ODCs) are constructed from SDCs.
- ☐ Controllability Don't Cares (CDCs) can be computed from internal SDCs and knowledge of any external network don't care patterns.
- ☐ In any multi-level Boolean network, it generally true that we extract all the implicit don't cares (CDCs and ODCs), no matter the size and complexity of the network.

 Question 4

Satisfiability Don't Cares (SDCs)

Consider this node computing the value X somewhere inside a Boolean logic network shown below. Which are the correct statements about the Satisfiability Don't Care SDC_X for the wire labeled X in this network?




- ☐ SDC_X includes the impossible patterns $Xabc = 1 - 0 -$, among others.
- ☐ SDC_X includes the impossible patterns $Xabc = 11 - -$, among others.
- ☐ SDC_X can be represented as $\bar{X}ab + \bar{X}b\bar{c} + X\bar{b} + X\bar{a}c$
- ☐ SDC_X is computed as $X \oplus (ab + b\bar{c})$
- ☐ SDC_X is a Boolean function of inputs X , a , b and c , which makes a 1 for impossible patterns of these variables.

 Question 5

Controllability Don't Cares (CDCs) in Multi-Level Logic

Consider this small Boolean logic network:



Use the methods from the lecture to extract the CDC_F patterns for node F .

Hint: You can use the **kbdd** BDD calculator to do this, if you want. This is, after all, *computational* Boolean algebra. The only tricky part is that you need to define the internal wires as *both* variables and functions. Since we already saw in lecture how

to compute the SDC for a node that is a simple OR gate, we can repeat the computation here for node Y , now done with **kbdd**:

```
boolean a b c Yvar
eval Ynode a + c
eval SDC_Y Ynode ^ Yvar
sop SDC_Y
```

Observe that we define “**Yvar**” so we can use it as a variable in the SDC computation, but we also define a function “**Ynode**” to compute “the expression for Y ”. We can then evaluate the SDC_Y cover, and can ask **kbdd** to print out an SOP form. **Kbdd** prints the following for “sop SDC_Y”:

```
KBDD: sop SDC_Y
  a & !Yvar
+ !a & c & !Yvar
+ !a & !c & Yvar
```

which is $a\bar{Y} + \bar{a}c\bar{Y} + \bar{a}\bar{c}Y$. Of course, this will not usually be optimized (i.e., a small equation). But you could use this as the start of a simple Kmap optimization to clean this up.


Which of the following statements are correct, in describing the CDC_F don't cares?

- ☐ There are 11 total impossible CDC patterns of $acXY$ for node F .
- ☐ Pattern $acXY = 00 --$ is impossible at the inputs to F .
- ☐ There are 10 total impossible CDC patterns of $(acXY)$ for node F .
- ☐ Pattern $acXY = 0001$ is impossible at the inputs to F .
- ☐ $CDC_F = (\forall b)[(Y \oplus (a + c) + X \oplus (ab + \bar{b}\bar{c})]$

 Question 6

Observability Don't Cares (ODCs) in Multi-Level Logic

Consider this small Boolean logic network:



Use the methods from the lecture to extract the ODC_F patterns for node F .

Hint: You can use the **kbdd** BDD calculator to do this, if you want. **Kbdd** has a very general mechanism to replace any variable in a function, with any arbitrary other function. (Example: take a piece of hardware with an output F and inputs a, b, c, d , and make a new piece of hardware with output G ; then connect the G output to the “ d ” input on F , replacing the variable “ d ” in F with the function G . It’s a very natural thing for hardware composition.) This also lets us cofactor things easily. Here is a small example, where we set function $F = x \oplus y \oplus z$ and then calculate the two Shannon cofactors $F(x=1)$ (which we call **F_x** in **kbdd**) and $F(x=0)$ (which we call **F_xbar** in **kbdd**):

```
KBDD: boolean x y z
KBDD: eval F x^y^z
F: x^y^z
KBDD: sop F
      x & y & z
+ x & !y & !z
+ !x & y & !z
+ !x & !y & z
KBDD: replace F_x F x 1
KBDD: sop F_x
      y & z
+ !y & !z
KBDD: replace F_xbar F x 0
```

KBDD: $\text{sop } F_{\text{xbar}}$

$y \& !z$

$+ !y \& z$

Which of the following statements are correct, in describing the ODC_F don't cares?

- ☐ Patterns $abcY = 10$ — — make all Z outputs insensitive to F .
- ☐ Patterns $abcY = 00$ — — make all Z outputs insensitive to F .
- ☐ $ODC_F = (\forall d)[\overline{(\partial Z1/\partial F)} \cdot \overline{(\partial Z2/\partial F)}]$
- ☐ There are 4 ODC patterns of $abcY$ for node F , that mask F at all Z outputs.
- ☐ There are 2 ODC patterns of $abcY$ for node F , that mask F at all Z outputs.

Question 7

Q7 LET'S TRY SIS!

The best way to understand what a real multi-level optimizer can do is to try it. So, let's go run **SIS** and see what happens. **SIS** is a multi-level logic synthesis tool originally developed at the University of California at Berkeley by many students working with Professors Bob Brayton and Alberto Sangiovanni-Vincentelli. A good reference about SIS is

<http://www.eecs.berkeley.edu/Pubs/TechRpts/1992/2010.html>

If you go look in the TOOLS section of our course website, you will find a short tutorial document about **SIS**. You run **SIS** exactly like you ran **ESPRESSO** in the last homework: you edit a small textfile with the right inputs; you upload it through our portal to the Coursera servers; we run it and send you back the results; you look at the results to answer this question. Please go look at the tutorial document before you proceed further in this problem.

Assuming you have read/viewed these tutorial materials, here is what we want you to do. Suppose we have two 3-bit unsigned integers, **a2 a1 a0** and **b2 b1 b0**. We want you to MULTIPLY these two numbers, and then compute the 4-bit result **s3 s2 s1 s0** modulo 13. So, think of this as the following computation:

$$s[3:0] = (a[2:0] * b[2:0]) \bmod 13$$

Keep in mind that you (conceptually) do the 3-bit multiply first to compute the **6-bit** product, then do the mod-13 remainder (a number between 0 and 12) as the result. If this was a C program, the inner loop would be something like:

```
unsigned int a, b s;
s = (a * b)%13;
s = s & 0x0000000f;
```

As one concrete example, if **a2 a1 a0 = 110** (the number 6), and **b2 b1 b0 = 101** (the number 5), then $6*5 = 30$, and $30 \bmod 13 = 4$ (since $30 = 2*13 + 4$). So the resulting 4-bit output is **s3 s2 s1 s0 = 0100**.

SIS can read many different input format, but in particular, it can read exactly the same truth table format (the so-called PLA format) that ESPRESSO can read. Since you already did a problem on the last assignment in this format, we will use this.

Do this: Make a file that describes this truth table. That file should start like this:

```
.i 6
.o 4
.ilb a2 a1 a0 b2 b1 b0
.ob s3 s2 s1 s0
```

And it should have lines that look this, for our $6*5 = 4 \bmod 13$:

```
110101 0100
```

We will use a standard synthesis script to optimize this result. Look at the SIS output and answer this question:

How many nodes are this Boolean logic network?

Question 8

(This question is a continuation of Question 7. Please refer to the description of the problem there).

How many literals are in this Boolean logic network?

(Hint: Literal is the appearance of variable in true or complemented form, which shows on the RHS of an "=" in any Boolean Logic node.)

Question 9

(This question is a continuation of Question 7. Please refer to the description of the problem there).

How many AND gates (product terms with at least 2 variables in them) are in this Boolean logic network?

☐ In accordance with the Honor Code, I certify that my answers here are my own work.

Submit Answers

Save Answers
